

Basic Electronics - 2

Hamtronics



Voltage and Resistance


Doc WA7PLC

November 2, 2020

@Sunlife ARC

Basic Electronics- Hamtronics Part 2

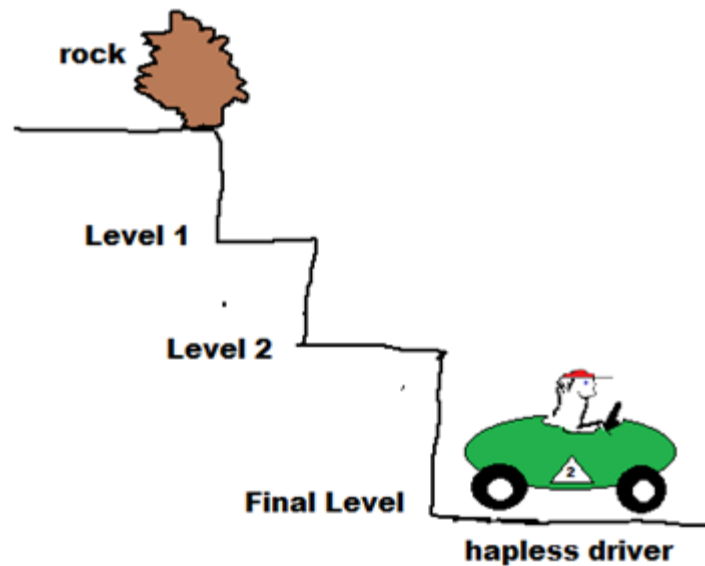- We will continue looking at voltage and resistance.
- First voltage ...




Remember voltage is energy/charge or
Joule/ Coulomb

So it is similar to a potential energy. With out
a current the voltage is there to work but
needs something to call it into use. Like a
rock on cliff above a car

Basic Electronics- Hamtronics Part 2

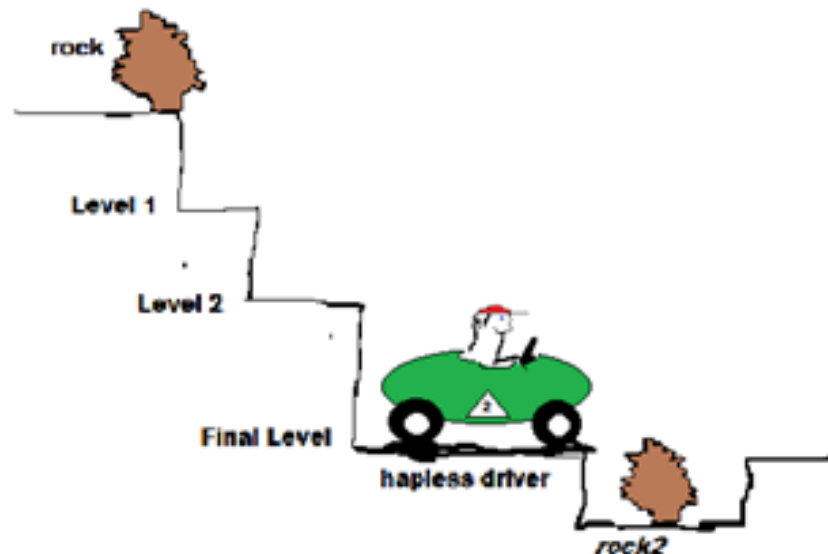- So the potential energy is positive. The energy can be viewed in 3 stages.




Here the rock 2 has negative energy. We must do work to move it up to the car. Slim chance the rock2 will spontaneously jump up to and hit the car.

Rock1 has positive energy with respect to ground and rock2 has negative energy with respect to ground!

So what, this is electronics!


Basic Electronics- Hamtronics Part 2

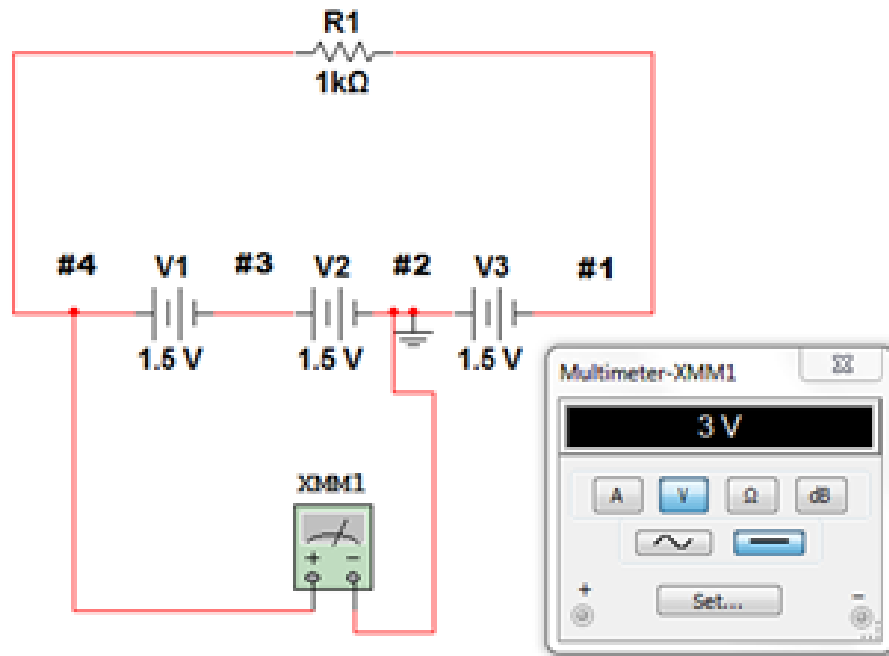- Kirchoff's Law is **Almost** as famous as Ohm's Law.
- Kirchoff states that voltages in series add.



Here the reading over two batteries is 3V.

Basic Electronics- Hamtronics Part 2

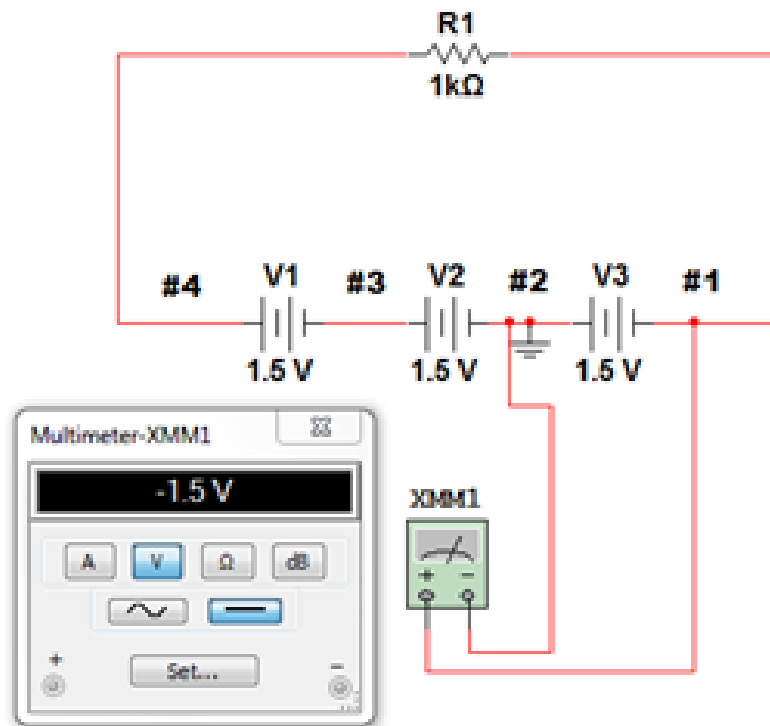

Note that the reading across the right hand battery is -1.5V


The negative value shows it is below ground. See the ground symbol between V2 and V3!

We usually measure volage with respect to where the neg (or black) lead of the meter to the ground of the circuit.

Analogous to the car sitting at ground.

Basic Electronics- Hamtronics Part 2

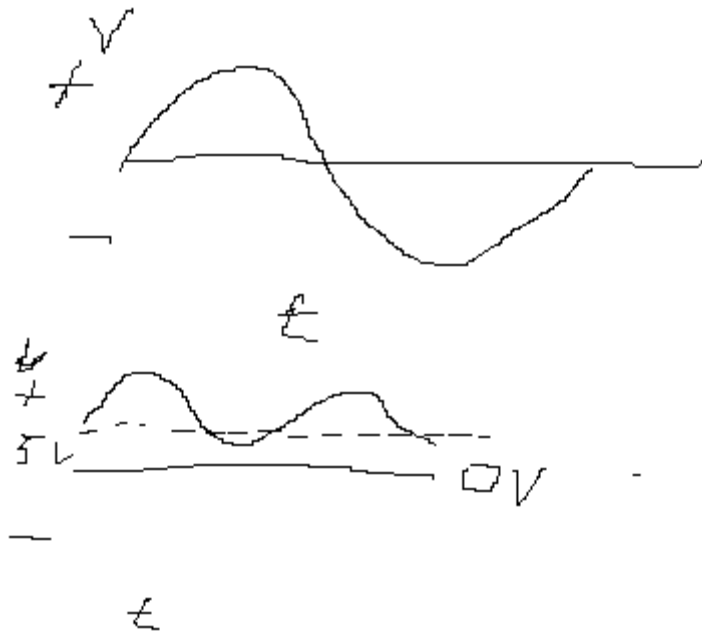□ So why do we want “dual polarity” power supplies?




With dual polarity we can have + and – values.

With single polarity our signal must ride on a DC level to avoid any – polarity.

Basic Electronics- Hamtronics Part 2

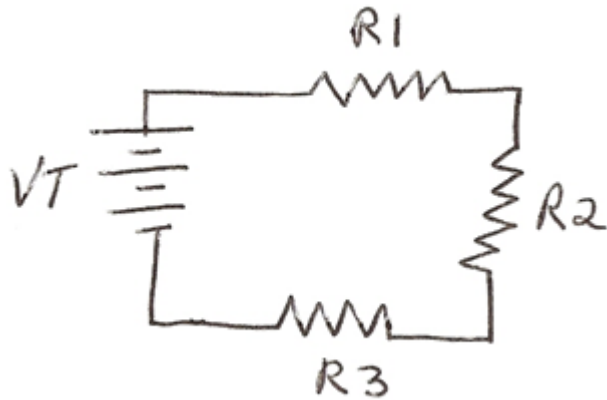- Now, lets look at resistors. Two possible wiring arrangements Series and Parallel.
- In series all the current goes through each resistor.




$$V_T = V_1 + V_2 + V_3$$

$$\text{But } I_1 = I_2 = I_3 = I_T$$

This is Kirchoff's Current Law


Basic Electronics- Hamtronics Part 2

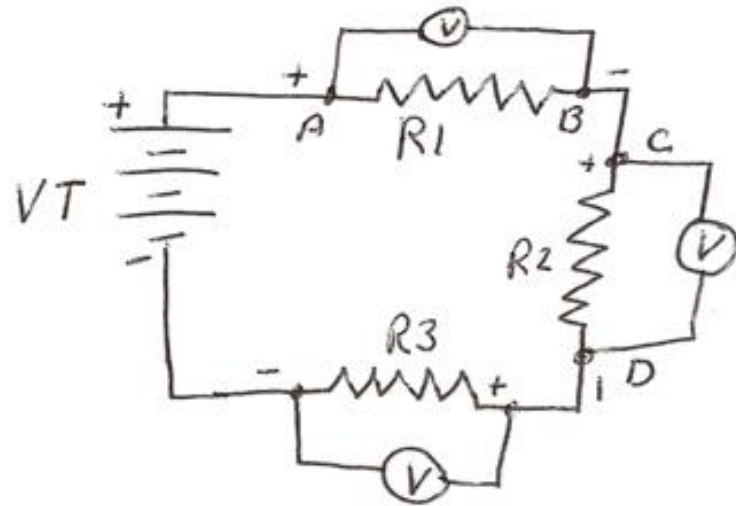

$$V_T = I \cdot R_1 + I \cdot R_2 + I \cdot R_3$$


$$I \cdot R_T = I \cdot R_1 + I \cdot R_2 + I \cdot R_3$$

$$R_T = R_1 + R_2 + R_3$$

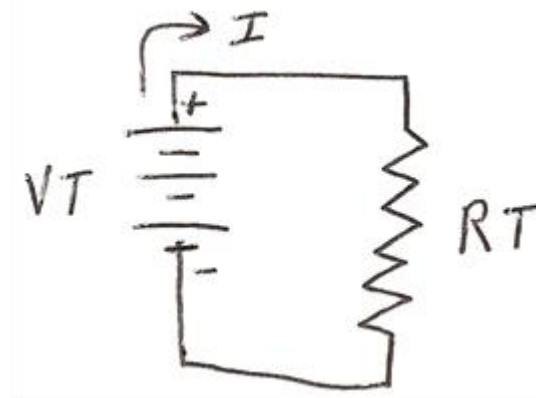

Basic Electronics- Hamtronics Part 2

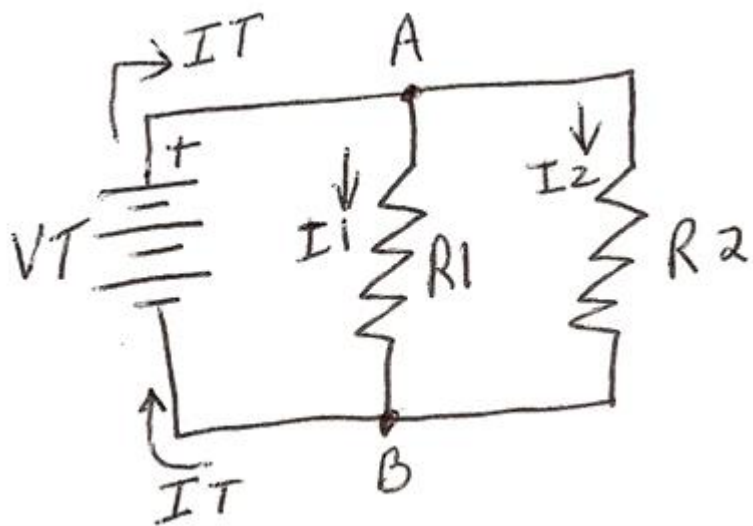- Now parallel circuits provide multiple paths for the current.



$$I_T = I_1 + I_2$$

Now it gets a bit complicated

Here $I_T = V_T/R_T$ and
 $I_T = I_1 + I_2$ so $\frac{V_T}{R_T} = \frac{V_T}{R_1} + \frac{V_T}{R_2}$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_T = \frac{R_1 * R_2}{R_1 + R_2} \quad (\text{or product /sum})$$

Basic Electronics- Hamtronics Part 2


□ Let's look at an example ... (with Smath)

Series

$$R1 := 1500 \quad R2 := 870 \quad R3 := 2500$$

$$RTs := R1 + R2 + R3$$

$$RTs = 4870$$

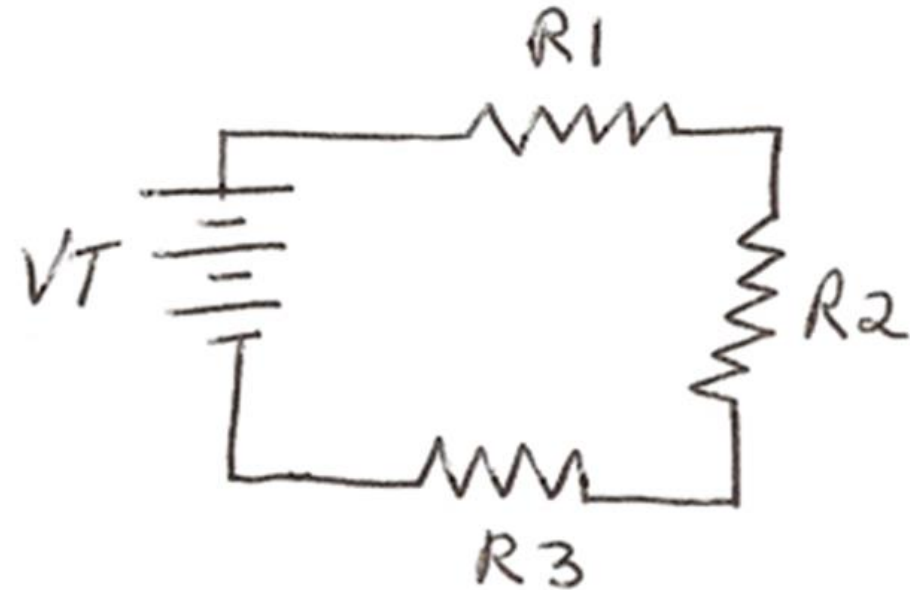

Basic Electronics- Hamtronics Part 2


□ Let's look at an example ... (with Smath)

Parallel

$$R1 := 1500 \quad R2 := 870$$

$$RTp := \frac{(R1 \cdot R2)}{R1 + R2}$$

$$RTp = 550.6329$$

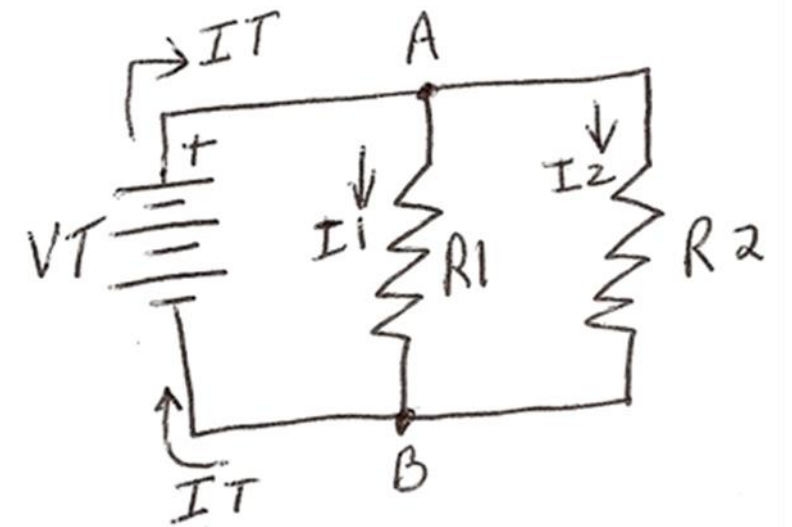

Basic Electronics- Hamtronics Part 2



Questions? Comments?

Doc WA7PLC

PLC@drcunningham.us

724-640-9143

www.drcunningham.us/hamtronics