

# Basic Electronics Part 4

## Phase and Resonance



- Hamtronics
- Basic Electronics Part 4
- "DOC" Cunningham  
WA7PLC
- January 18, 2021
- @Sunlife ARC

# **Basic Electronics Part 4**

## **Phase and Resonance**



**Let's have a quick review of C and L and R**

**ELI the ICE MAN**

**This means - - -**

**Voltage leads current in an inductor and ...**

**Current leads Voltage in a capacitor! This is  
with respect to the resistor value.**

# Basic Electronics Part 4

## Phase and Resonance

**Resonance occurs when the capacitive reactance in the circuit exactly matches the inductive reactance. Or  $X_C = X_L$**


$$X_C := \frac{1}{2 \cdot \pi \cdot f \cdot C} \quad X_L := 2 \cdot \pi \cdot f \cdot L$$

$$\frac{1}{2 \cdot \pi \cdot f \cdot C} = 2 \cdot \pi \cdot f \cdot L$$

$$f_r := \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$

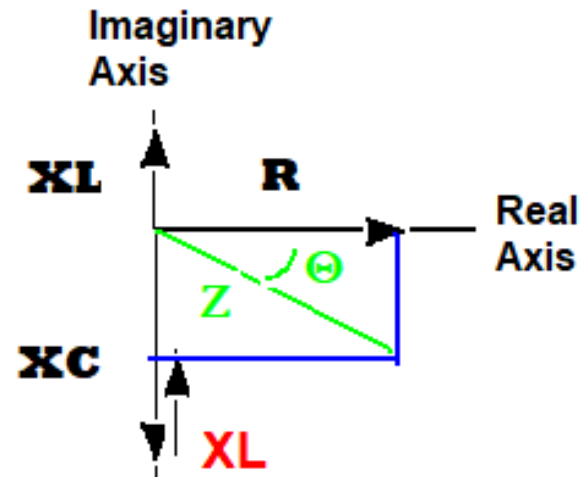**We represent the XC as lagging (-90 deg) and the XL as Leading (+90 deg)**

**Since Current leads voltage in XC then Voltage lags current  
This is a voltage plot.**



**This allows us to use math to predict the values of Z and the phase shift that results.**

# Basic Electronics Part 4

## Phase and Resonance


The way to look at it is using *Phasors*

A phasor is a vector showing the relationship of the value of the reactance and its “phase angle” with respect to each other and any circuit resistance. The phasors are shown with their voltage relationships

Both  $X_C$  and  $X_L$  are called the imaginary value of the Impedance,  $Z$

$$Z := R + i \cdot (X_C - X_L)$$

$$i := \sqrt{-1}$$

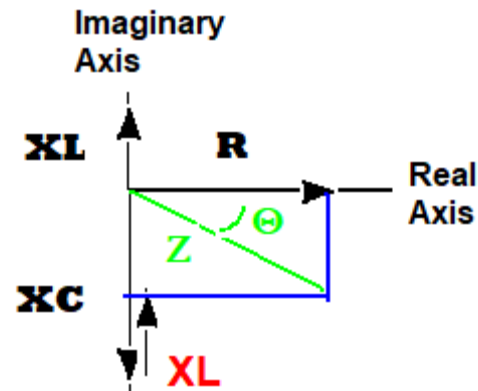

# **Basic Electronics Part 4**

## **Phase and Resonance**



**First off, do not let the term “imaginary” throw you off. This is a mathematical way to deal with the shift that these active devices introduce to the AC signal.**

**There is nothing imaginary about an imaginary number. The problem comes from the existence of the square root of -1 in the definition of the XC and XL values.**

**Luckily Smath will do all the math for you – If needed.**

# Smath for non-resonance

$$C := 0.5 \cdot 10^{-6}$$

$$R := 5000$$

$$L := 3$$

$$f := 60$$

$$X_C := \frac{1}{2 \cdot \pi \cdot f \cdot C}$$

$$X_C = 5305.1648$$

$$X_L := 2 \cdot \pi \cdot f \cdot L$$

$$X_L = 1130.9734$$

$$\text{Imaginary} := X_L + (-X_C)$$


$$\text{Imaginary} = -4174.1914$$

$$Z := \sqrt{R^2 + \text{Imaginary}^2}$$


$$Z = 6513.3612$$

$$\text{TANGENT}\theta := \frac{\text{Imaginary}}{R}$$

$$\text{TANGENT}\theta = -0.8348$$

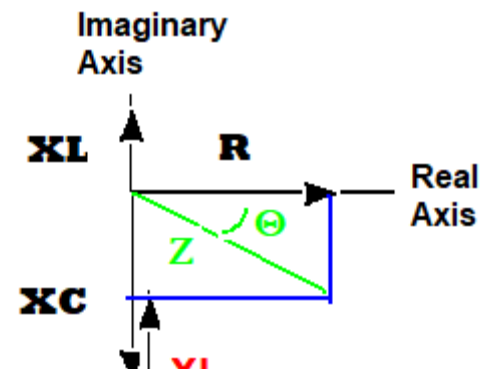

# Smath Angle Calculations

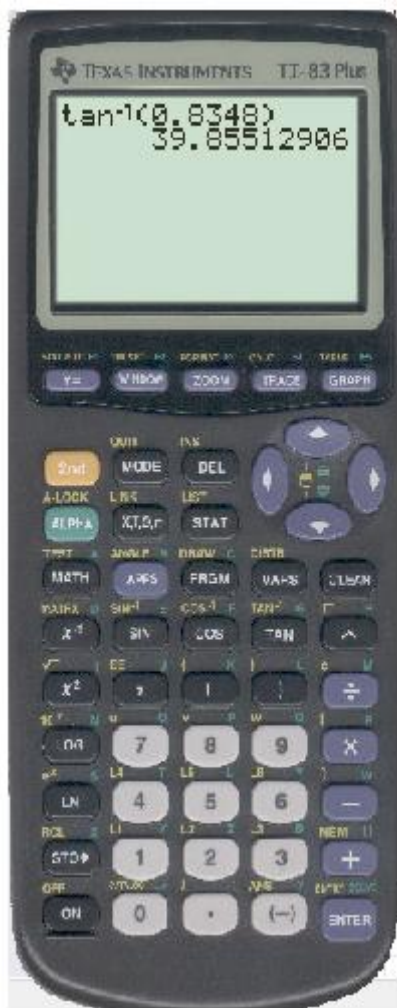

Here we use a calculator to find the arctan or  $\tan^{-1}(0.8348)$  which gives 39 degrees.

This type of calculation is involved in the Extra Class exam. Those questions are easier to understand with this background.

For a reference see a recent Math section of CQ Magazine.




# Basic Electronics Part 4

## Phase and Resonance

**Back to resonance conditions...**

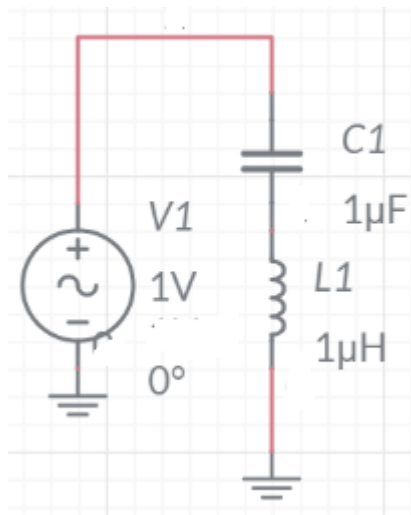**At resonance, the pair of C and L have no effective resistance Each cancelling the reactance of the other.**

At resonance the  $f_r$  resonance frequency is



$$L := 1 \cdot 10^{-6} \quad \text{Henries}$$


$$C := 1 \cdot 10^{-6} \quad \text{Farad}$$

$$f_r := \frac{1}{2 \cdot \pi \cdot \sqrt{L \cdot C}}$$

$$f_r = 1.5915 \cdot 10^5 \quad \text{Hertz}$$

# Basic Electronics Part 4

## Phase and Resonance

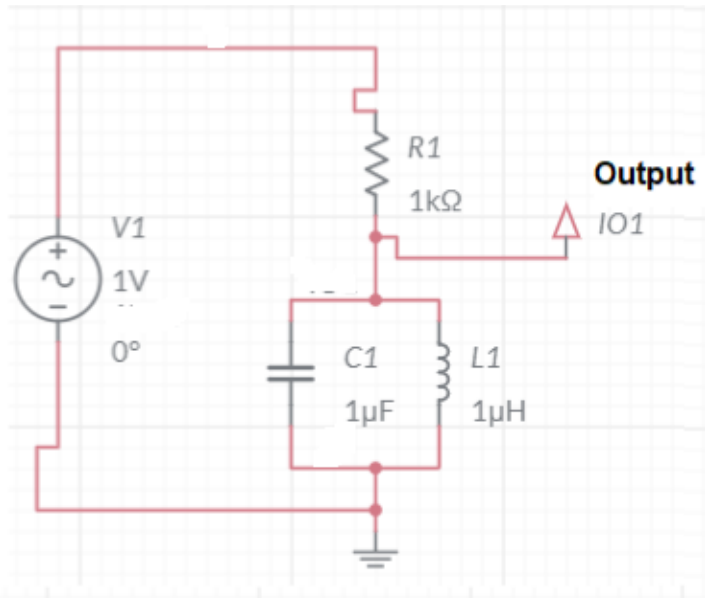


**This means**  
 **$Z = V_{\text{source}} / I_{\text{source}}$**   
 **$Z = V_{\text{source}} / 0 = \text{Infinite Ohms}$**   
**Or high impedance!**

**The calculation is the same.**

**At resonance the reactance of the combination goes toward infinity... To see this, consider the current in the coil and the capacitor are 180 degrees out of phase. So the net draw from the source is zero. But the voltage is the same. Hence the voltage from the source is seen by the load. In resonance the coil and cap pass the current back and forth to each other.**

# Tuned Circuit Radio

All sorts of frequencies

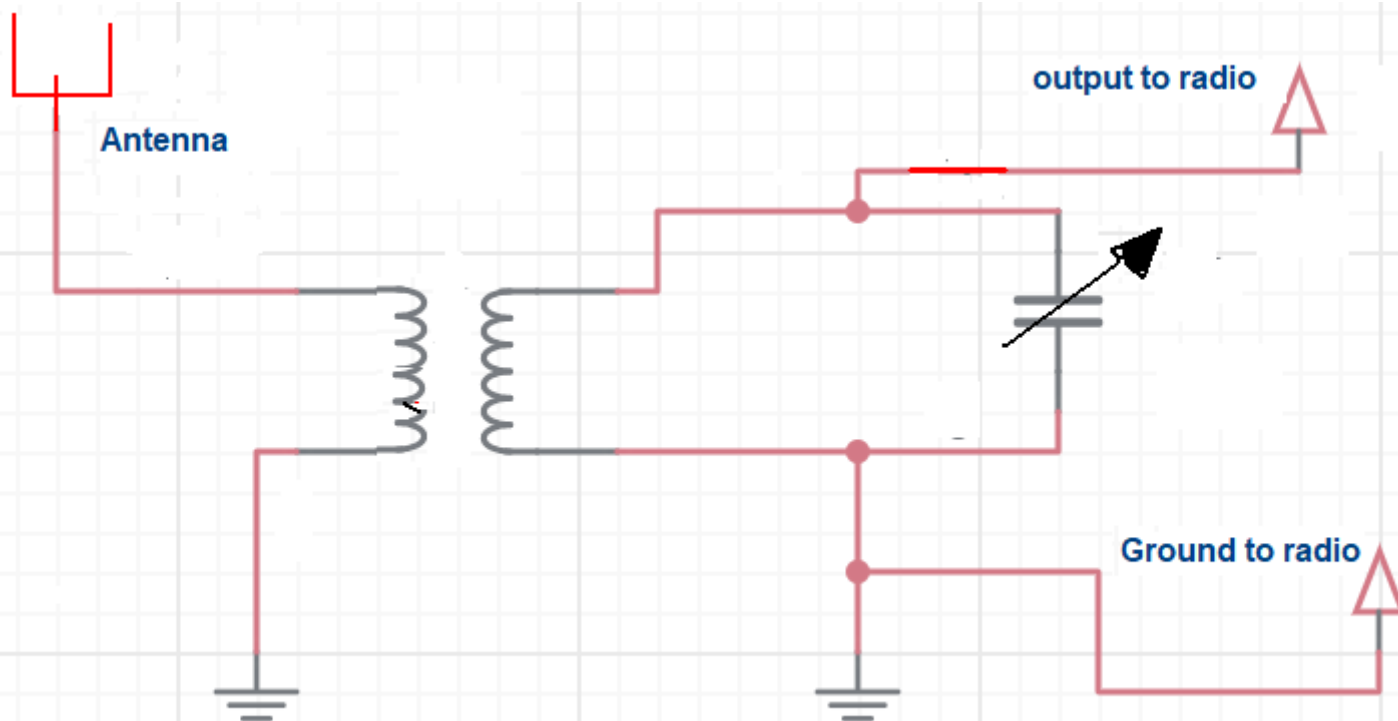

**When tuned the resistance of the circuit is huge and the voltage is at the resonant freq. This is passed on to the detector stages eventually the amplifier stages.**

# Basic Electronics Part 4

## Phase and Resonance

In a transmitter the operation can be the same.

More on this topic when we look at receives and transmitters. Coming soon to a Zoom near you. Now its time for Coffee.



Comments on this or other presentations send to  
**PLC @ drcunningham.us**  
Also, topics to consider for future presentations in coming years.

## Questions?

[www.drcunningham.us/hamtronics](http://www.drcunningham.us/hamtronics)